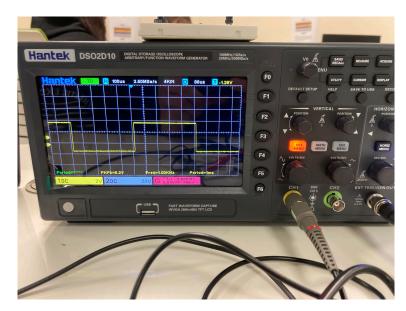



${\rm ENGS152~Circuits~Lab~Section~B} \\ {\rm RC,~RL~and~RLC~circuit~time~domain~analysis}$

Mher Saribekyan Nina Prazyan


March 6, 2025



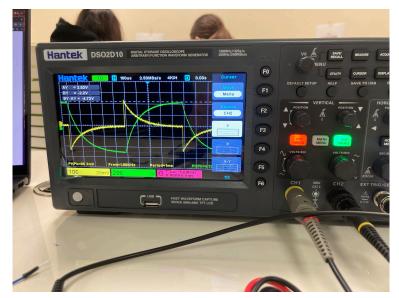
$$\tau = RC \implies R = \frac{\tau}{C} = \frac{0.1 \cdot 10^{-3}}{100 \cdot 10^{-9}} = 1k\Omega$$




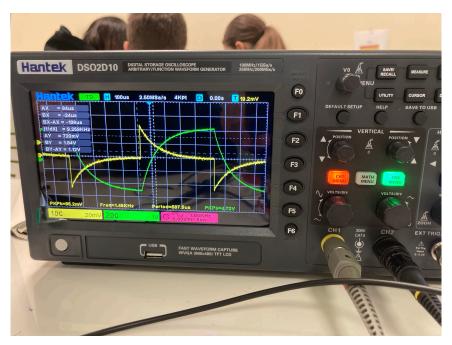Peak to peak voltage is 4.72V. 63% gives around 0.7736V compared to ground. The time measured gives $108\mu S$, which matches our time constant.




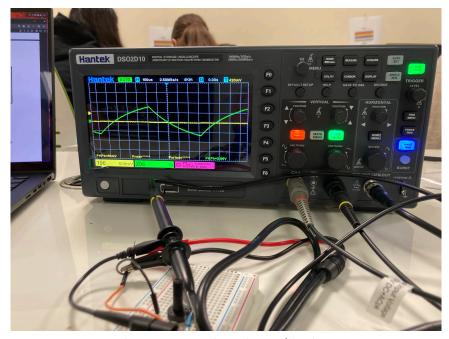

High resistance, slow charge/discharge.

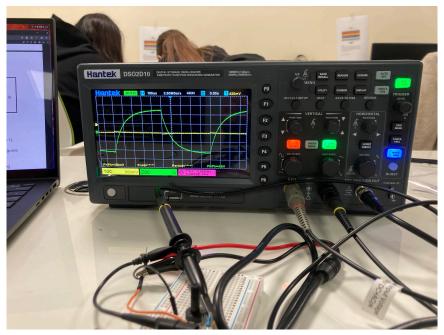


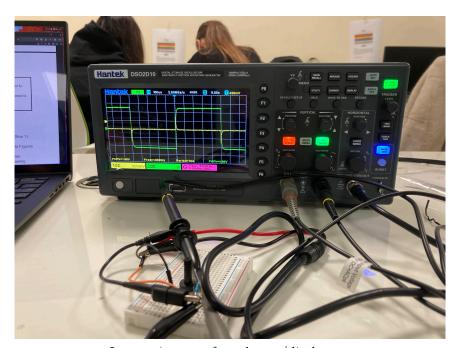
Medium resistance, medium charge/discharge.




Low resistance, fast charge/discharge.

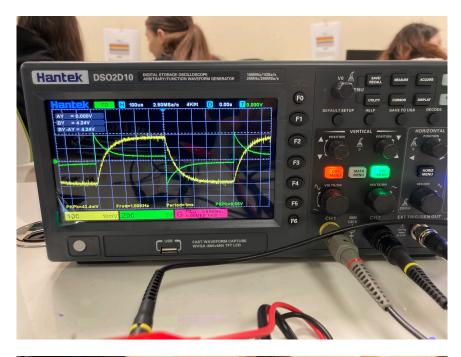
$$\tau = \frac{L}{R} \implies R = \frac{L}{\tau} = \frac{100 \cdot 10^{-3}}{0.1 \cdot 10^{-3}} = 1k\Omega$$



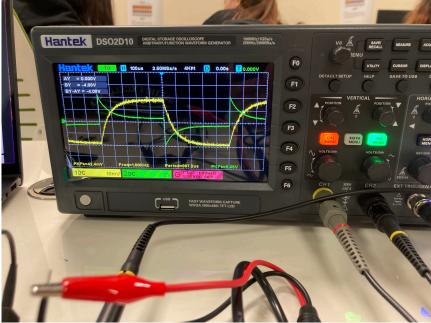


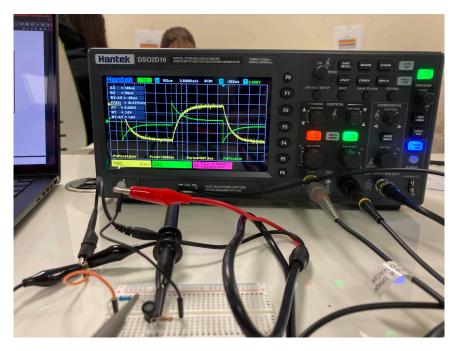Peaks are at around +4.24V and -4.08V. The 37% charge is at around 1.57V, which we measure at $96\mu S$.




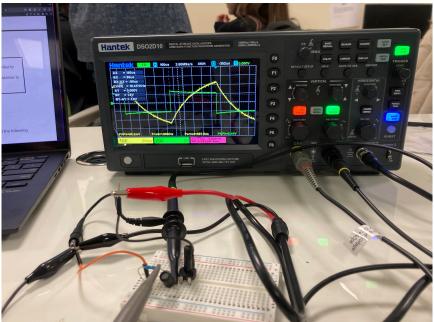


High resistance, slow charge/discharge.

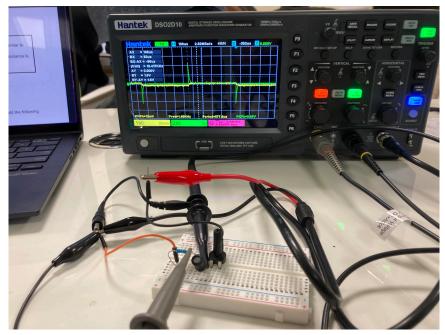


Low resistance, fast charge/discharge.

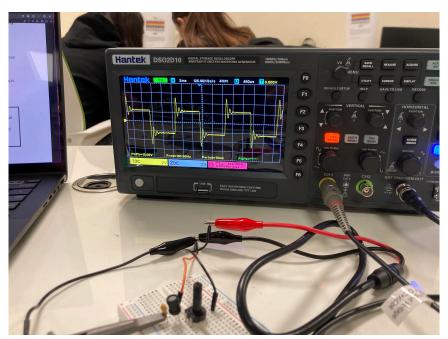

Underdamped RLC

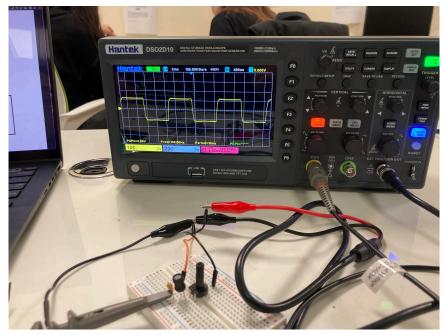

Critically damped RLC

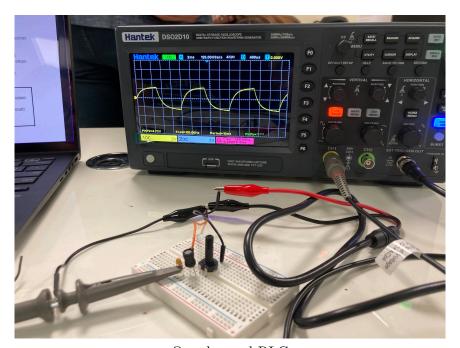

Overdamped RLC