



Digital version

ENGS152 Circuits Lab Section A

RL and RC Frequency Domain Analysis

Mher Saribekyan Nina Prazyan

March 21, 2025

Step 1: Signal Analysis

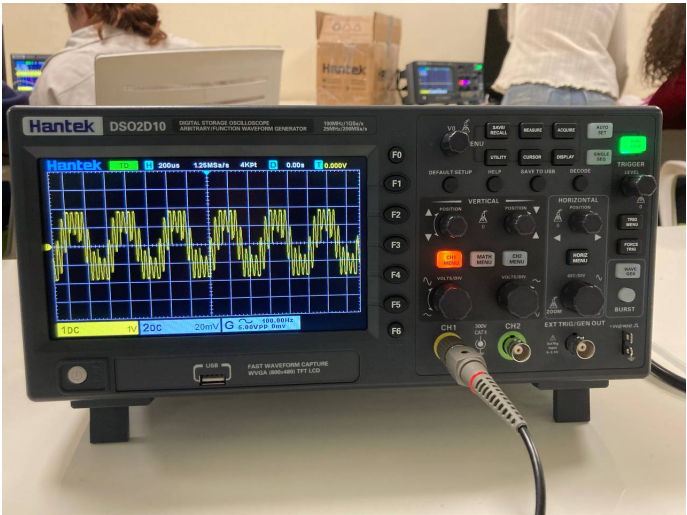


Figure 1: Sound wave on the scope

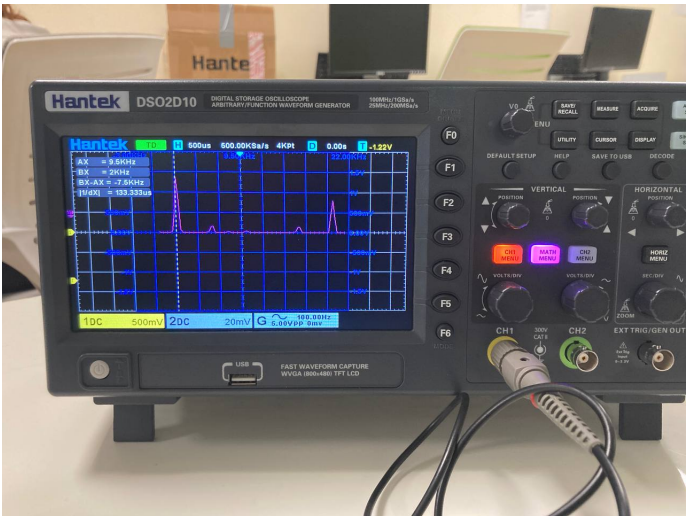


Figure 2: Singnal FFT 2khz peak

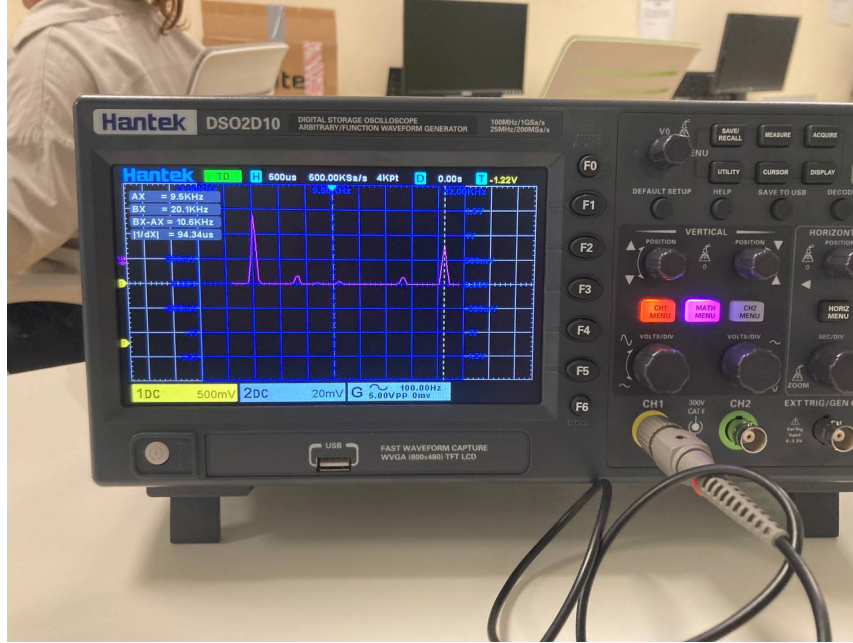


Figure 3: Signal FFT 20khz peak

Step 2: First order low-pass filter

RL low pass was chosen, with a cutoff frequency of about $5 - 6kHz$, however due to the limited values of components, $8kHz$ was chosen. The calculated values for the resistor and inductor are $R = 5.1k\Omega$ and $I = 100mH$, therefore $f_{cutoff} = \frac{R}{2\pi L} \approx 8kHz$.

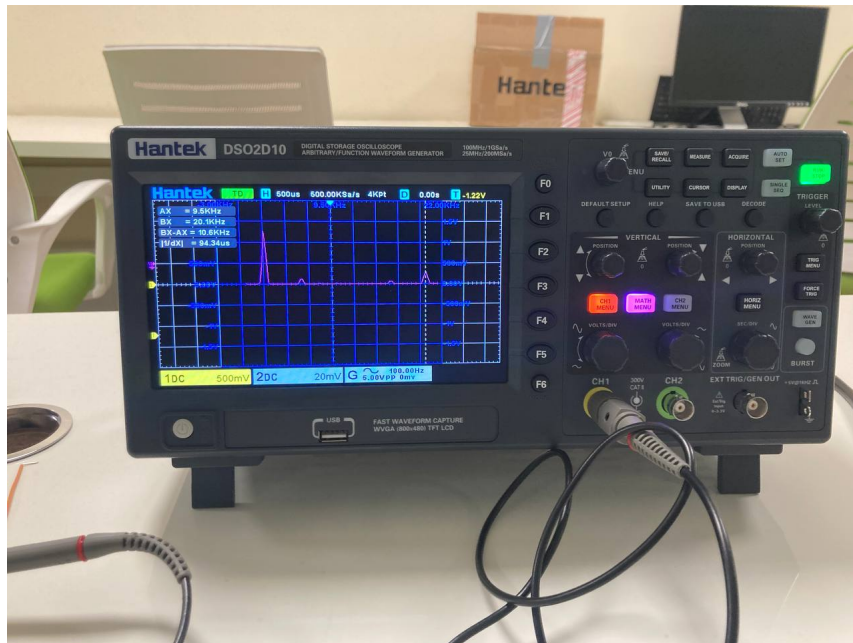


Figure 4: First order low-pass in FFT

The $20kHz$ peak is a lot lower than in **Figure 2**, from around $0.9V$ to around $0.3V$.

Step 3: Second order low-pass filter

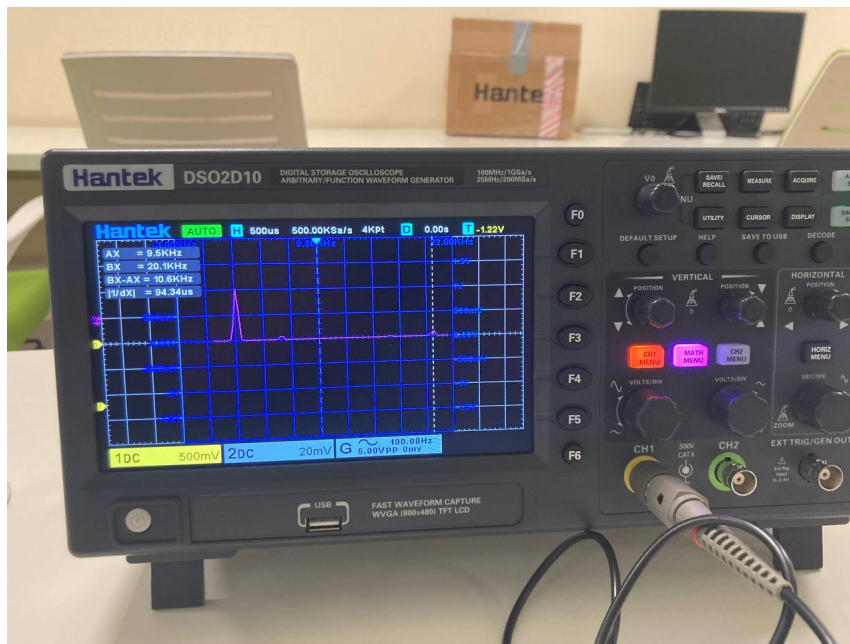


Figure 5: Second order low-pass in FFT

The 20kHz peak is a lot lower than in **Figure 4**, about 0.1V, therefore it is a more effective filter.

Step 4: First order high-pass filter

RC high pass was chosen, with a cutoff frequency of about 18kHz, however due to the limited values of components, 16kHz was chosen. The calculated values for the resistor and capacitor are $R = 10k\Omega$ and $C = 1nF$, therefore $f_{\text{cutoff}} = \frac{1}{2\pi RC} \approx 16\text{kHz}$.

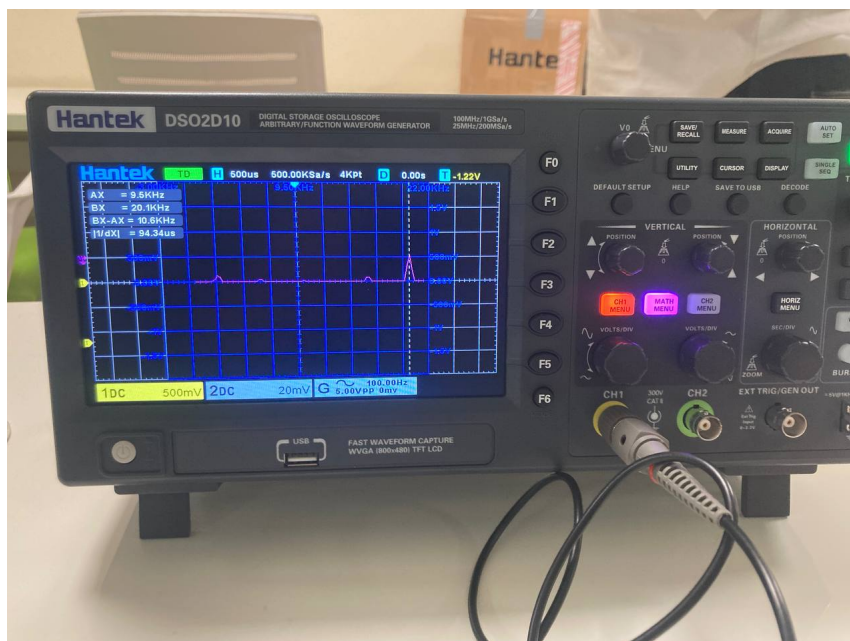


Figure 6: First order high-pass in FFT

The 2kHz peak is a lot lower than in **Figure 2**, from around 1.4V to around 0.2V .

Step 5: Second order high-pass filter

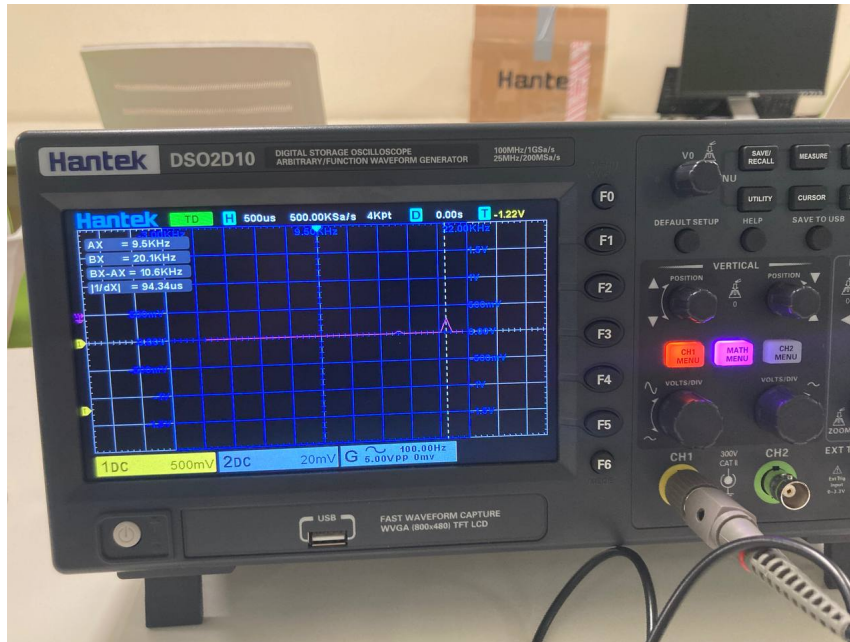


Figure 7: Second order high-pass in FFT

The 2kHz peak is filtered so much, that it is not measurable, therefore it is a more effective filter.



Figure 8: A nice drawing of a sunny beach