



Digital version

# ENGS254 Signals and Systems Lab


## RC lowpass

Mher Saribekyan A09210183

April 24, 2026

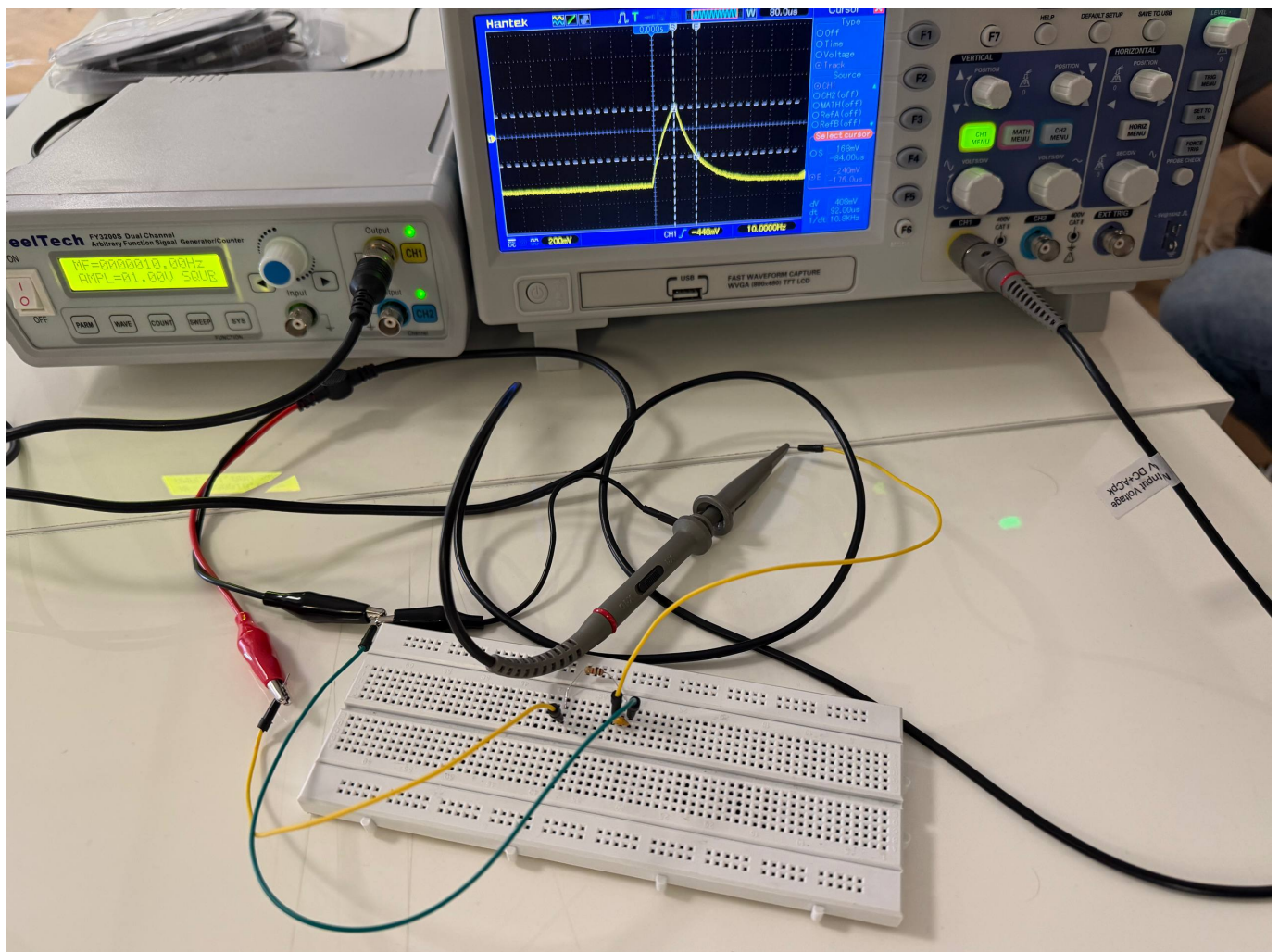
### RC discharge and cut-off frequency

RC circuit was constructed, impulse signal was supplied and the output was measured to find the cut-off frequency at 0.707 point point of the RC discharge curve.




We get  $94\mu s$ , which gives us cut-off frequency of  $10.6kHz$ . Theoretical cut-off frequency is  $f = \frac{1}{2\pi RC} = \frac{1}{2\pi \cdot 10^3 \cdot 10^{-8}} \approx 15.9kHz$ .
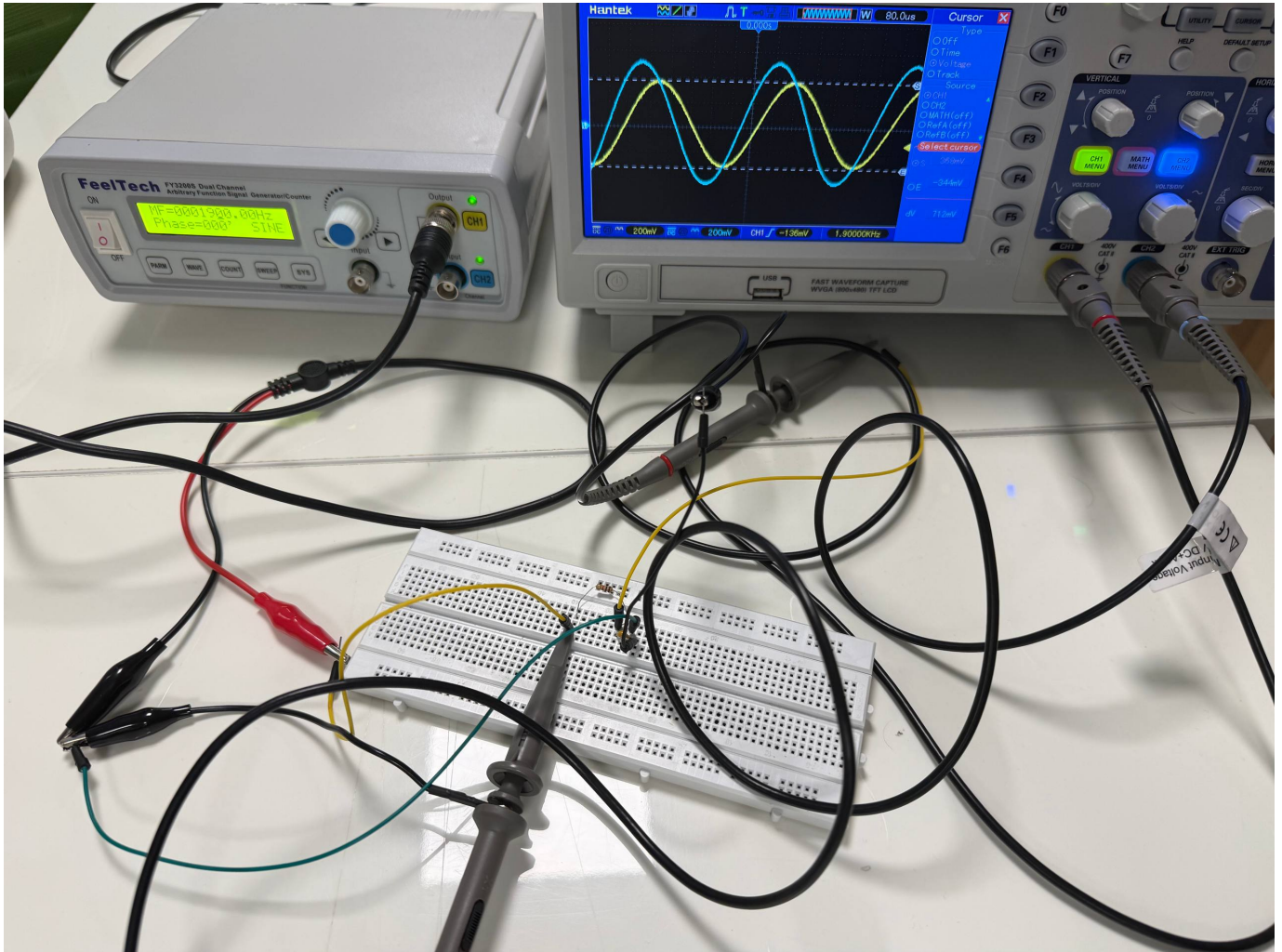
## Different input frequencies and cut-off frequency



Capacitor was replaced with a  $100nF$  one. Sine waves of different frequency and  $1V$  amplitude were supplied. At the frequency of around  $1.9kHz$ , we get around  $0.707$  gain. Theoretical cut-off frequency is  $f = \frac{1}{2\pi RC} = \frac{1}{2\pi \cdot 10^3 \cdot 10^{-7}} \approx 1.59kHz$ .

## FFT and cut-off frequency

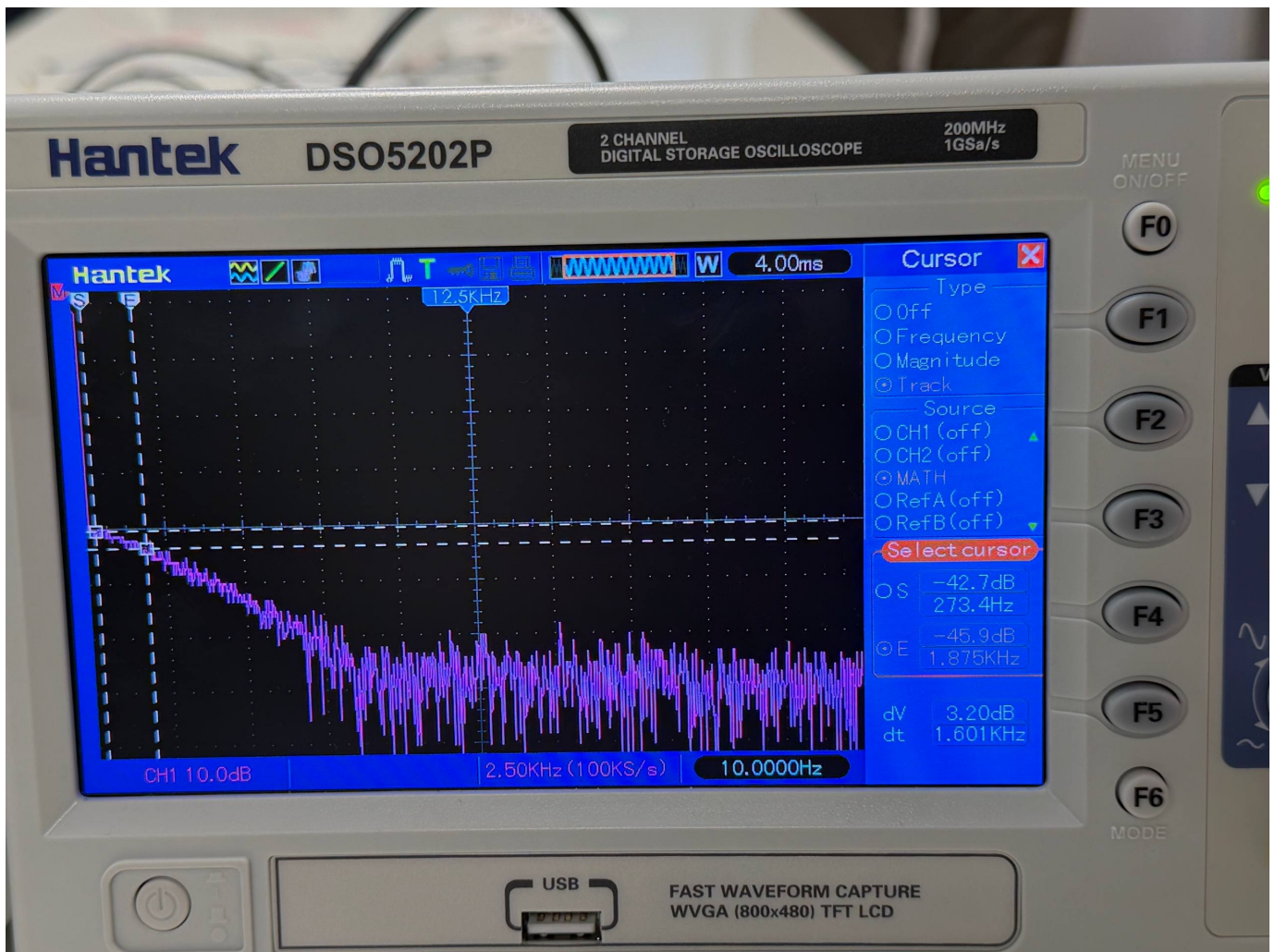

Impulse was given and FFT was calculated on the output. By finding the 0.707 gain point from the FFT we get a cutoff frequency of  $1.6\text{kHz}$ .